

Electricity

- 1) Electricity - Form of energy involves an electrical charge.
- 2) Static electricity - electricity at rest.
- 3) Current electricity - electrical charge in motion.
- 4) Charge - a property attributed a matter such as electrons are negative and protons are positive.
- 5) Effect of Charges ;
 - ① like charges repel each other.
 - ② unlike charges attract each other.
 - ③ imbalance of protons and electrons create a charge.
- 6) Electrical conductors - matter that will allow the transfers of electrical energy, Ex: metals
- 7) Electrical insulators - matter that will not allow the transfer of electrical energy, Ex: Rubber
- 8) Induced charge - transfer of electrons from one object to another can charge an object.
- 9) Electric field - deals with the properties of charges that always exists in the space around a charged particle.

10) Electrical potential energy - the ability to move an electric charge from one point to another and is dependant on its position in an electric field.

11) Potential difference - the change in the electrical potential energy of a charged particle divided by its charge and occurs as a charge moves from one place to another in an electric field.

12) Voltage - SI unit for potential difference and is equal to 1 Joule/Coulomb.
Note: Pressure on the electric charge in an electric circuit.

13) Electric current - rate at which the charges move through the wire.

14) Ampere - one coulomb of charge moving past a point in 1 second.

15) Resistance - Caused by internal friction, which slows the movement of charges through a conducting material.

16) Ohm's Law - resistance is equal to the voltage divided by the Amperage of a system.

17 Ohm's Law Calculations:

$$R = \frac{V}{I}$$

$$R = \text{electrical resistance} = \text{Ohm} = \frac{\text{Js}}{\text{C}^2} = \Omega$$

$$V = \text{Voltage} = \frac{\text{J}}{\text{C}}$$

$$I = \text{Ampereage} = A = \frac{\text{C}}{\text{S}}$$

Example #1 $R = \text{---}$ $V = 120\text{V}$ $I = 10\text{A}$

$$= 120 \frac{\text{J}}{\text{C}} \quad = 10 \frac{\text{C}}{\text{S}}$$

$$R = \frac{V}{I} = \frac{120 \frac{\text{J}}{\text{C}}}{10 \frac{\text{C}}{\text{S}}} = \left(120 \frac{\text{J}}{\text{C}} \right) \left(\frac{\text{S}}{10 \text{C}} \right) = 12 \frac{\text{Js}}{\text{C}^2} = 12 \Omega$$

Example #2 $R = 0.256 \Omega$ $V = \text{---}$ $I = 5.00\text{A}$

$$= 0.256 \frac{\text{Js}}{\text{C}^2} \quad = 5.00 \frac{\text{C}}{\text{S}}$$

$$R = \frac{V}{I}$$

$$V = I R = \left(5.00 \frac{\text{C}}{\text{S}} \right) \left(0.256 \frac{\text{Js}}{\text{C}^2} \right) = 1.28 \frac{\text{J}}{\text{C}} = 1.28 \text{V}$$

Example #3 $R = 0.512 \Omega$ $V = 210\text{V}$ $I = \text{---}$

$$= 0.512 \frac{\text{Js}}{\text{C}^2} \quad = 210 \frac{\text{J}}{\text{C}}$$

$$R = \frac{V}{I}$$

$$I = \frac{V}{R} = \frac{210 \frac{\text{J}}{\text{C}}}{0.512 \frac{\text{Js}}{\text{C}^2}} = \left(210 \frac{\text{J}}{\text{C}} \right) \left(\frac{\text{C}^2}{0.512 \text{Js}} \right) = 4.10 \times 10^3 \frac{\text{C}}{\text{S}} = 4.10 \times 10^3 \text{A}$$

18) Comparing Resistances of materials

- 1) Conductors have low resistance.
(Look at atom's electron cloud looseness.)
- 2) Insulator have high resistance.
(Atom's electron cloud is tight.)


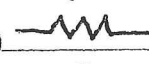




19) Semi conductors - material that has properties that can act as an insulator in one situation and a conductor in another.

20) Electric circuit - a complete path for the electric charge to travel.
Electrical source \rightarrow Conductor (wire) \rightarrow switch \rightarrow wire \rightarrow Load (light bulb) \rightarrow wire \rightarrow Electrical source.

21) Closed circuit - a complete path.

22) Open Circuit - No complete path.

23) Schematic diagram - this depicts the construction of an electric circuit.

- 24) Schematic Symbols
- | | | |
|----|---|------------------|
| 1) |  | - Conductor |
| 2) |  | - Resistor |
| 3) |  | - light bulb |
| 4) |  | - Current source |
| 5) |  | open - Switch |
| 6) |  | closed |


25) Series Circuit - Electrical devices are connected with only one path for the current to flow.

Example:



26) Parallel circuit - Electrical devices are connected with each device having its own path for the current to flow.

Example:

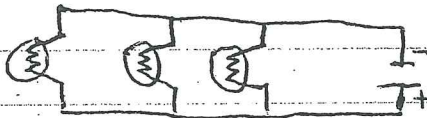

27) Electrical power - the rate at which electrical energy is changed.

28) Electrical Power Calculation:

$$P = V I$$

$$P = \text{Power} = \frac{J}{s} = \text{Watt}$$

$$V = \text{Voltage} = \frac{J}{C}$$

$$I = \text{Ampere} = \frac{C}{s} = A$$

28) Example #1 $P = \underline{\hspace{2cm}}$ $V = 220\text{V}$ $I = 10.0\text{A}$
 $= 220 \frac{\text{J}}{\text{C}}$ $= 10.0 \frac{\text{C}}{\text{s}}$

$$P = VI = \left(220 \frac{\text{J}}{\text{C}} \right) \left(10.0 \frac{\text{C}}{\text{s}} \right) = 2200 \frac{\text{J}}{\text{s}} = 2200\text{W}$$

Example #2 $P = 60.0\text{W}$ $V = \underline{\hspace{2cm}}$ $I = 5.00\text{A}$
 $= 60.0 \frac{\text{J}}{\text{s}}$ $= 5.00 \frac{\text{C}}{\text{s}}$

$$P = VI$$

$$V = \frac{P}{I} = \frac{60.0 \frac{\text{J}}{\text{s}}}{5.00 \frac{\text{C}}{\text{s}}} = \left(60.0 \frac{\text{J}}{\text{s}} \right) \left(\frac{\text{s}}{5.00 \text{C}} \right) = 12.0 \frac{\text{J}}{\text{C}} = 12.0\text{V}$$

Example #3 $P = 50.0\text{W}$ $V = 110\text{V}$ $I = \underline{\hspace{2cm}}$
 $= 50.0 \frac{\text{J}}{\text{s}}$ $= 110 \frac{\text{J}}{\text{C}}$

$$P = VI$$

$$I = \frac{P}{V} = \frac{50.0 \frac{\text{J}}{\text{s}}}{110 \frac{\text{J}}{\text{C}}} = \left(50.0 \frac{\text{J}}{\text{s}} \right) \left(\frac{\text{C}}{110 \text{J}} \right) = .455 \frac{\text{C}}{\text{s}} = .455\text{A}$$

29) Relationships with Ohm's law and Electrical Power

$$1) R = \frac{V}{I}$$

$$P = VI$$

$$V = IR$$

$$V = \frac{P}{I}$$

$$I = \frac{V}{R}$$

$$I = \frac{P}{V}$$

30) (A) $V = IR$ $V = \frac{P}{I}$ Relationship P, R, I

$V = V$

$IR = \frac{P}{I}$ $\therefore P = RI^2$

(B) $I = \frac{V}{R}$ $I = \frac{P}{V}$ Relationship P, R, V

$I = I$

$\frac{V}{R} = \frac{P}{V}$ $\therefore P = \frac{V^2}{R}$

31) Fuse and Circuit Breaker - device that prevents too many amperes of current from passing through a circuit.

32) Wire gauge - size of the wire and it help determine how many amperes of current can pass through safely.

